

Work each of the following problems. SHOW ALL WORK.


4. An electric saw at a local hardware store features a motor that supplies 15 A. Find the resistance of the saw when it is plugged into a 110 V outlet.

5. Defibrillator machines are used to deliver an electric shock to the human heart and resuscitate a heart that has stopped beating. A current as low as 18 mA can trigger resuscitation. Using 95 k Ω as the resistance, determine the minimum output voltage needed by a defibrillator for it to be effective.

6. A taser sends about 1100 V through the human body, resulting in an average current of 2.5 mA. Using these numbers, estimate the electrical resistance of the human body.

Work each of the following problems. SHOW ALL WORK.

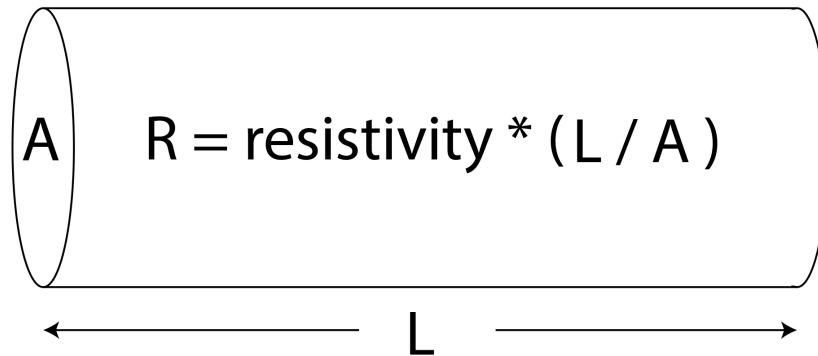7. Resistivity indicates the overall resistance of a material. It is measured by units of Ωm and depends on material type. To determine the resistivity of a wire, divide its length by its area as indicated in the diagram below:



The wire heating element of an electric toaster is 190 cm long with a diameter of 0.05 cm. If the heating element is made of nichrome, which has a resistivity of $1.1 \times 10^{-6} \Omega\text{m}$, what is its overall resistance?

8. You are analyzing an electrical circuit around a battery with a 9 V output. The circuit is designed to carry a maximum current of 2 A. Anything above that and a fuse in the circuit will blow out to keep the circuit from being overloaded. Currently, a 3.2Ω appliance is the only resistor in the circuit. Will the fuse blow out? If so, what resistance is needed to stay below the 2 A limit?

Name:

Date:

Work each of the following problems. SHOW ALL WORK.

9. A lamp draws a current of 0.34 A from a power outlet that supplies 120 V. What is the resistance of the lamp?