

Work each of the following problems. SHOW ALL WORK.

1. How much current is flowing through a wire if 21.5 C of charge passes a point in 6.3 seconds?

$$q = 21.5 \text{ C}$$

$$t = 6.3 \text{ s}$$

$$I = \frac{q}{t}$$

$$I = \frac{21.5 \text{ C}}{6.3 \text{ s}}$$

$$I = 3.4 \text{ A}$$

2. A 210Ω resistor is connected in a circuit with a 110 V battery. How much charge passes through a point in the circuit in two minutes?

$$R = 210 \Omega$$

$$V = 110 \text{ V}$$

$$t = 2 \text{ min} = 120 \text{ s}$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{110 \text{ V}}{210 \Omega}$$

$$I = 0.52 \text{ A} = 0.52 \text{ C/s}$$

$$(0.52 \text{ C/s})(120 \text{ s}) = 63 \text{ C of charge}$$

3. How long would these devices need to be in operation before 1,000,000 C of charge passes through them?

- a. LED night light ($I = 0.0041 \text{ A}$)

$$t_{LED} = \frac{1 \times 10^6 \text{ C}}{0.0041 \text{ A}} = 2.4 \times 10^8 \text{ s} = 68,000 \text{ hours}$$

$$I = \frac{q}{t}$$

- b. incandescent night light ($I = 0.052 \text{ A}$)

$$t_{inl} = \frac{1 \times 10^6 \text{ C}}{0.052 \text{ A}} = 1.9 \times 10^7 \text{ s} = 5,300 \text{ hours}$$

$$It = q$$

$$It = 1 \times 10^6 \text{ C}$$

$$t = \frac{1 \times 10^6 \text{ C}}{I}$$

- c. 60 W incandescent light bulb ($I = 0.4 \text{ A}$)

$$t_{60W} = \frac{1 \times 10^6 \text{ C}}{0.4 \text{ A}} = 2.5 \times 10^6 \text{ s} = 690 \text{ hours}$$

- d. large light fixture ($I = 2.1 \text{ A}$)

$$t_{fixture} = \frac{1 \times 10^6 \text{ C}}{2.1 \text{ A}} = 4.8 \times 10^5 \text{ s} = 130 \text{ hours}$$

questions continued on next page

Unit 5E_Practice Problems TEACHER

Work each of the following problems. **SHOW ALL WORK.**

4. An electric saw at a local hardware store features a motor that supplies 15 A. Find the resistance of the saw when it is plugged into a 110 V outlet.

$$V = 110 \text{ V}$$

$$I = 15 \text{ A}$$

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{110 \text{ V}}{15 \text{ A}}$$

$$R = 7.3 \Omega$$

5. Defibrillator machines are used to deliver an electric shock to the human heart and resuscitate a heart that has stopped beating. A current as low as 18 mA can trigger resuscitation. Using 95 k Ω as the resistance, determine the minimum output voltage needed by a defibrillator for it to be effective.

$$I = 18 \text{ mA} = 0.018 \text{ A}$$

$$R = 95 \text{ k}\Omega = 95,000 \Omega$$

$$V = IR$$

$$V = (0.018 \text{ A})(95,000 \Omega)$$

$$V = 1710 \text{ V}$$

6. A taser sends about 1100 V through the human body, resulting in an average current of 2.5 mA. Using these numbers, estimate the electrical resistance of the human body.

$$V = 1100 \text{ V}$$

$$I = 2.5 \text{ mA} = 0.0025 \text{ A}$$

$$V = IR$$


$$R = \frac{V}{I}$$

$$R = \frac{1100 \text{ V}}{0.0025 \text{ A}}$$

$$R = 440,000 \Omega = 440 \text{ k}\Omega$$

Work each of the following problems. **SHOW ALL WORK.**

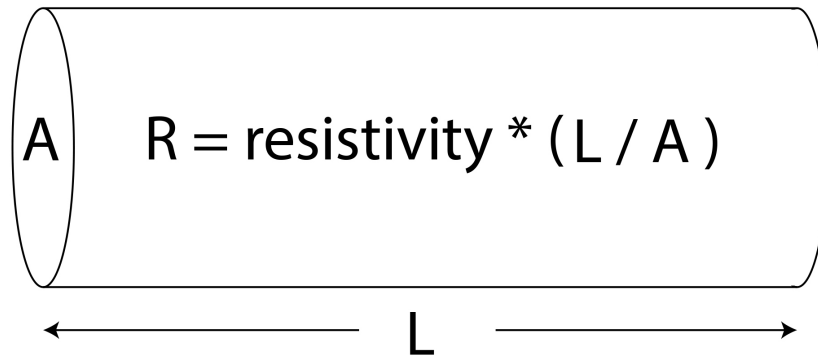7. Resistivity indicates the overall resistance of a material. It is measured by units of Ωm and depends on material type. To determine the resistivity of a wire, divide its length by its area as indicated in the diagram below:



The wire heating element of an electric toaster is 190 cm long with a diameter of 0.05 cm. If the heating element is made of nichrome, which has a resistivity of $1.1 \times 10^{-6} \Omega m$, what is its overall resistance?

$$\text{resistivity} = 1.1 \times 10^{-6} \Omega m$$

$$L = 190 \text{ cm} = 1.9 \text{ m}$$

$$D = 0.05 \text{ cm} = 0.0005 \text{ m}$$

$$A = \pi \left(\frac{D}{2} \right)^2 = 3.14159 \left(\frac{0.0005 \text{ m}}{2} \right)^2 = 2.0 \times 10^{-7} \text{ m}^2$$

$$R = \text{resistivity} \left(\frac{L}{A} \right)$$

$$R = 1.1 \times 10^{-6} \Omega m \left(\frac{1.9 \text{ m}}{2.0 \times 10^{-7} \text{ m}^2} \right)$$

$$R = 10.5 \Omega$$

Work each of the following problems. SHOW ALL WORK.

8. You are analyzing an electrical circuit around a battery with a 9 V output. The circuit is designed to carry a maximum current of 2 A. Anything above that and a fuse in the circuit will blow out to keep the circuit from being overloaded. Currently, a 3.2Ω appliance is the only resistor in the circuit. Will the fuse blow out? If so, what resistance is needed to stay below the 2 A limit?

$$V = 9V$$

$$R = 3.2 \Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{9V}{3.2 \Omega}$$

$$I = 2.8 A$$

Yes, the fuse will blow out under this current load.

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{9V}{2A}$$

$$R = 4.5 \Omega$$

9. A lamp draws a current of 0.34 A from a power outlet that supplies 120 V. What is the resistance of the lamp?

$$I = 0.34 A$$

$$V = 120 V$$

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{120V}{0.34A}$$

$$R = 353 \Omega$$