

Work each of the following problems. SHOW ALL WORK.

1. A microwave oven has a power rating of 1,200 W. If it receives 120 V of potential difference, what is the current in the microwave?

$$P = IV$$
$$1200 \text{ W} = I(120 \text{ V})$$
$$I = 10 \text{ A}$$

2. Using the information from the previous question, what is the resistance of the microwave?

$$V = IR$$
$$120 \text{ V} = (10 \text{ A})R$$
$$R = 12 \Omega$$

3. What is the resistance in the filament of a 60 W light bulb that receives 120 V of potential difference?

$$P = \frac{V^2}{R}$$
$$60 \text{ W} = \frac{(120 \text{ V})^2}{R}$$
$$60 \text{ W} = \frac{14400 \text{ V}^2}{R}$$
$$R = \frac{14400 \text{ V}^2}{60 \text{ W}}$$
$$R = 240 \Omega$$

4. The current running through a toaster oven is 7.5 A when it is connected to 120 V of potential difference. What is the power rating of the toaster?

$$P = IV$$
$$P = (7.5 \text{ A})(120 \text{ V})$$
$$P = 900 \text{ W}$$

Work each of the following problems. **SHOW ALL WORK.**

5. Two resistors, one with $6\ \Omega$ of resistance and the other with $8\ \Omega$ of resistance, are connected in series to a $9\ \text{V}$ battery. How much power is dissipated by these two resistors?

$$R_{eq} = R_1 + R_2$$

$$R_{eq} = 6\ \Omega + 8\ \Omega$$

$$R_{eq} = 14\ \Omega$$

$$P = \frac{V^2}{R}$$

$$P = \frac{(9\ \text{V})^2}{14\ \Omega}$$

$$P = \frac{81\ \text{V}^2}{14\ \Omega}$$

$$P = 5.8\ \text{W}$$

6. If the two resistors from the previous question were arranged in parallel, how much power would they dissipate?

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{6\ \Omega} + \frac{1}{8\ \Omega}$$

$$\frac{1}{R_{eq}} = \frac{4}{24\ \Omega} + \frac{3}{24\ \Omega}$$

$$\frac{1}{R_{eq}} = \frac{7}{24\ \Omega}$$

$$\frac{R_{eq}}{1} = \frac{24\ \Omega}{7}$$

$$R_{eq} = 3.43\ \Omega$$

$$P = \frac{V^2}{R}$$


$$P = \frac{(9\ \text{V})^2}{3.43\ \Omega}$$

$$P = \frac{81\ \text{V}^2}{3.43\ \Omega}$$

$$P = 23.62\ \text{W}$$

Work each of the following problems. **SHOW ALL WORK.**

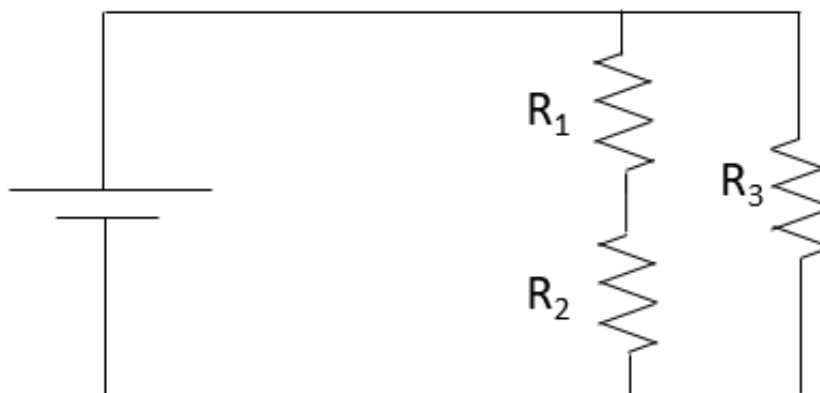7. Each resistor in the circuit diagram below has a resistance of $2\ \Omega$. If the potential difference supplied by the batteries in the circuit is $6\ \text{V}$, how much power is dissipated?



$$R_{1+2} = R_1 + R_2$$

$$R_{1+2} = 2\ \Omega + 2\ \Omega$$

$$R_{1+2} = 4\ \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_{1+2}} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{4\ \Omega} + \frac{1}{2\ \Omega}$$

$$\frac{1}{R_{eq}} = \frac{1}{4\ \Omega} + \frac{2}{4\ \Omega}$$

$$\frac{1}{R_{eq}} = \frac{3}{4\ \Omega}$$

$$\frac{R_{eq}}{1} = \frac{4\ \Omega}{3}$$

$$R_{eq} = 1.33\ \Omega$$

$$P = \frac{V^2}{R}$$

$$P = \frac{(6\ \text{V})^2}{1.33\ \Omega}$$

$$P = \frac{36\ \text{V}^2}{1.33\ \Omega}$$

$$P = 27\ \text{W}$$

Work each of the following problems. **SHOW ALL WORK.**

8. How many joules of energy are needed to keep a 45 W ceiling fan working for 6 hours?

$$6 \text{ hours} = 360 \text{ minutes} = 21600 \text{ seconds}$$

$$P = \frac{\Delta E}{t}$$

$$45 \text{ W} = \frac{\Delta E}{21600 \text{ s}}$$

$$\Delta E = 972000 \text{ J}$$

9. How much does it cost to power a refrigerator for 30 days if it is rated at 200 W and the power company charges \$0.07 per kWh?

$$30 \text{ days} = 720 \text{ hours}$$

$$200 \text{ W} = 0.2 \text{ kW}$$

$$P = \frac{\Delta E}{t}$$

$$0.2 \text{ kW} = \frac{\Delta E}{720 \text{ h}}$$

$$\Delta E = 144 \text{ kWh}$$

$$\frac{144 \text{ kWh}}{1} \times \frac{\$0.07}{1 \text{ kWh}} = \$10.08$$